

# **Multi-Level Logic Optimization - Node Optimization**

# Simplification

---

- Represent each node in two level form
- Use espresso to minimize each node
- Several simplification procedures which vary only in the size of don't care constructed
  - don't care set empty
  - subset of don't care

# Simplification

---

Don't care

- External DC
- Internal DC (derived from the structure)
  - (1) Satisfiability DC (SDC)
  - (2) Observability DC (ODC)

# Satisfiability Don't Care

---

- Satisfiability DC (to all nodes)

Ex:  $x = ab$

$$y = a'b'$$


$$f = x'y' + a$$

$$\therefore x \oplus ab = x(ab)' + x'(ab)$$

- Why?

Expand the Boolean space of PI to include intermediate variables  $B^n \rightarrow B^{n+m}$

$n=2 \ m=1$

 

In general,  $SDC = \sum (y_i \cdot f_i' + y_i' \cdot f_i)$

# Observability Don't Care

---

- Observability DC ( to certain intermediate node)

$\frac{\delta f}{\delta x}$  f is sensitive to the value of x

$(\frac{\delta f}{\delta x})'$  f is not sensitive to the value of x  
x is observable at f if  $\frac{\delta f}{\delta x} \neq 0$

(Note  $\frac{\delta f}{\delta x}$  is a function of the inputs)

## Example


---

Ex:

$$u = ab + xc' + x'b'$$

$$x = a'b + ac'$$
 
$$\left(\frac{\delta u}{\delta x}\right)' = u_x \bullet u_{x'} + u_x' \bullet u_{x'}'$$



$$u_x = ab + c'$$

$$u_{x'} = ab + b'$$

$$\begin{aligned} \left(\frac{\delta u}{\delta x}\right)' &= u_x \bullet u_{x'} + u_x' \bullet u_{x'}' \\ &= (ab + b'c') + a'b'c \quad (\text{the ODC of } x) \end{aligned}$$

$$u = ab + xc' + x'b'$$

$$a=1 \ b=1 \quad \Rightarrow u = 1 \cdot 1 + xc' + x'b' = 1$$

$$b=0 \ c=0 \quad \Rightarrow u = a \cdot 0 + x \cdot 1 + x' \cdot 1 = 1$$

$$a=0 \ b=1 \ c=1 \quad \Rightarrow u = 0 \cdot 1 + x \cdot 0 + x' \cdot 0 = 0$$

# Observability Don't Care

---

- ODC relative to  $x$  is

$$\text{ODC}_x = \prod_{f_i \in \text{output}} \left( \frac{\partial f_i}{\partial x} \right)'$$

- Including the external DC

$$\prod_{f_i \in \text{output}} \left( \left( \frac{\partial f_i}{\partial x} \right)' + D_{xi} \right)$$

- In general, the complete DC is too large  
solutions:

filter the DC

=> subset “support” filter

# Standard Script of SIS

---

sweep                      constant propagation, remove buffer  
eliminate -l              collapse; node has < 1000 cubes  
simplify                   espresso for each node  
eliminate -l

sweep  
eliminate 5              value > 5  
simplify

resub -a                   algebraic div  
gkx -abt 30              -a generate all kernel -b the best kernel inter  
                             -t value saved

resub -a; sweep  
gcx -bt 30               -b the best cube -t the value saved  
resub -a; sweep

gkx -abt 10  
resub -a; sweep  
gcx -bt 10  
resub -a; sweep

.....



# **Boolean Difference and ODC for Logic Network of Simple Gates**

# Controlling and Non-controlling Values of Simple Gates


---

- Given a **simple gate** (i.e. AND, OR, NAND, NOR), a **controlling** value on an input determines the output of the gate independent of the other inputs
- Given a **simple gate** (i.e. AND, OR, NAND, NOR), a **non-controlling** value on an input cannot determine the output of the gate independent of the other inputs
- Example:
  - 0 is a controlling value for AND gate  
1 is non-controlling value for AND gate
  - 0 is a controlling value for NAND gate  
1 is non-controlling value for NAND gate
  - 1 is a controlling value for OR gate  
0 is non-controlling value for OR gate
  - 1 is a controlling value for NOR gate  
0 is non-controlling value for NOR gate

 
# Boolean Difference of Simple Gates

---

- Non-controlling value of a side input is merely a specialization of the Boolean difference of an on-input to the simple gate
- $a$  is an on-input and  $b$  is a side input



$$\frac{\partial f}{\partial a} = b$$

 

$$\frac{\partial g}{\partial a} = \bar{b}$$

## ODC of Simple Gates

---


- Controlling value of a side input is merely a specialization of ODC of an on-input to the simple gate
- $a$  is an on-input and  $b$  is a side input



- ODC = complement of Boolean difference

# Example of Computing Boolean Difference of *ff*


---

 

- $(C = 0 \text{ and } D=x) \text{ or } (C = x \text{ and } D=0)$   
 $\Rightarrow C' + D'$
- $E = 1$   
 $\Rightarrow E$
- Boolean Difference (*ff*) =  $(C' + D') E$   
(conditions of side inputs are *anding*)

## Example of Computing ODC of *ff*

---

 


- $(C = 1 \text{ and } D=1)$   
 $\Rightarrow CD$
- $E = 0$   
 $\Rightarrow E'$
- $ODC(ff) = CD + E'$  (conditions of side inputs are *oring*)
- $(ODC(ff))' = \text{Boolean Difference } (ff)$   
 $= (C' + D')E$

# Incompleteness of Don't Cares

---

- Example

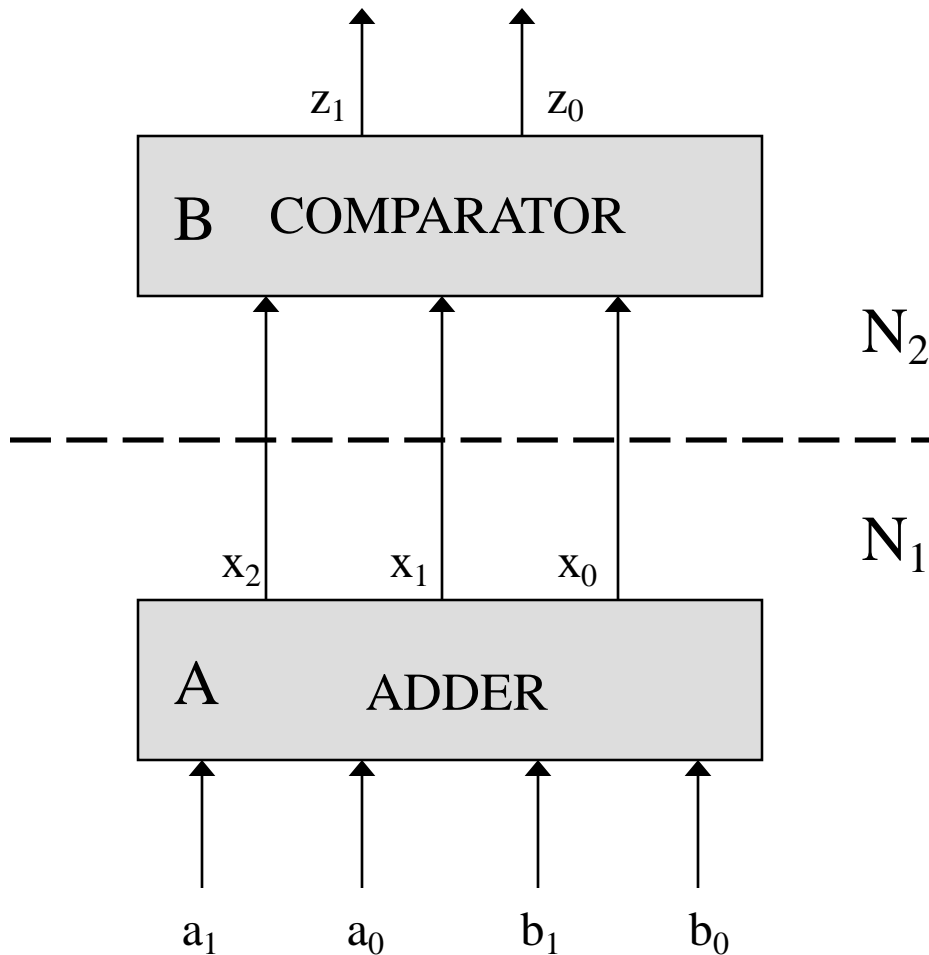

$$Z = 01 \Rightarrow a + b < 3$$

$$Z = 00 \Rightarrow a + b = 3$$

$$Z = 10 \Rightarrow a + b > 3$$

## Equivalence

---

$x_2$	$x_1$	$x_0$	$z_1$	$z_0$
0	0	0	0	1
0	0	1	0	1
0	1	0	0	1
0	1	1	0	0
1	0	0	1	0
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

Input values 000, 001, and 010 are equivalent with respect to ***B***.

{000,001,010} forms an equivalence class.

The other equivalent classes are:

{011} and {100,101,110,111}



## Boolean Relation Formulation

---

If  $x'$ ,  $x''$  are input values indistinguishable from the outputs of  $\mathbf{B}$ , they are interchangeable output values for  $\mathbf{A}$ .

$a_1$	$a_0$	$b_1$	$b_0$	$x_2$	$x_1$	$x_0$
0	0	0	0	{000,001,010}		
0	0	0	1	{000,001,010}		
0	0	1	0	{000,001,010}		
0	1	0	0	{000,001,010}		
1	0	0	0	{000,001,010}		
0	0	1	1	{011}		
0	1	0	1	{000,001,010}		
0	1	1	0	{011}		
1	0	0	1	{011}		
1	0	1	0	{100,101,110,111}		
1	1	0	0	{011}		
0	1	1	1	{100,101,110,111}		
1	0	1	1	{100,101,110,111}		
1	1	0	1	{100,101,110,111}		
1	1	1	0	{100,101,110,111}		
1	1	1	1	{100,101,110,111}		

## Example

---

The optimal implementation of the following relation  $R \subseteq B^2 \times B^2$

a	b	x	y
0	0	0 0	0 1
0	1	0 1	1 0
1	1	1 1	
1	0	1 0	

	a	0	1
b			
0		00	10
1		01	11


	a	0	1
b			
0		00	10
1		10	11

	a	0	1
b			
0		01	10
1		01	11

	a	0	1
b			
0		01	10
1		10	11

# Problems

---

 

1. How to find a multiple-output sub-network ?
2. How to utilize Boolean Relations for minimization ?
  - full set of Boolean Relation
  - subset of Boolean Relation