

Multi-Level Logic Optimization

Multi-Level Logic Synthesis

- Two Level Logic :

$$\begin{aligned} F1 &= \bar{x}yz\bar{w} + \bar{x}y\bar{z}\bar{w} + xyzw + xy\bar{z} \\ &= \bar{x}y\bar{w} + xyzw + xy\bar{z} \end{aligned}$$

- Espresso
- Programmable Logic Array (PLA)



- Multilevel Logic :

$$F2 = g(a + b\bar{c}) + c$$



- Standard Cell

Multi-level Logic





- Standard cell implementation:

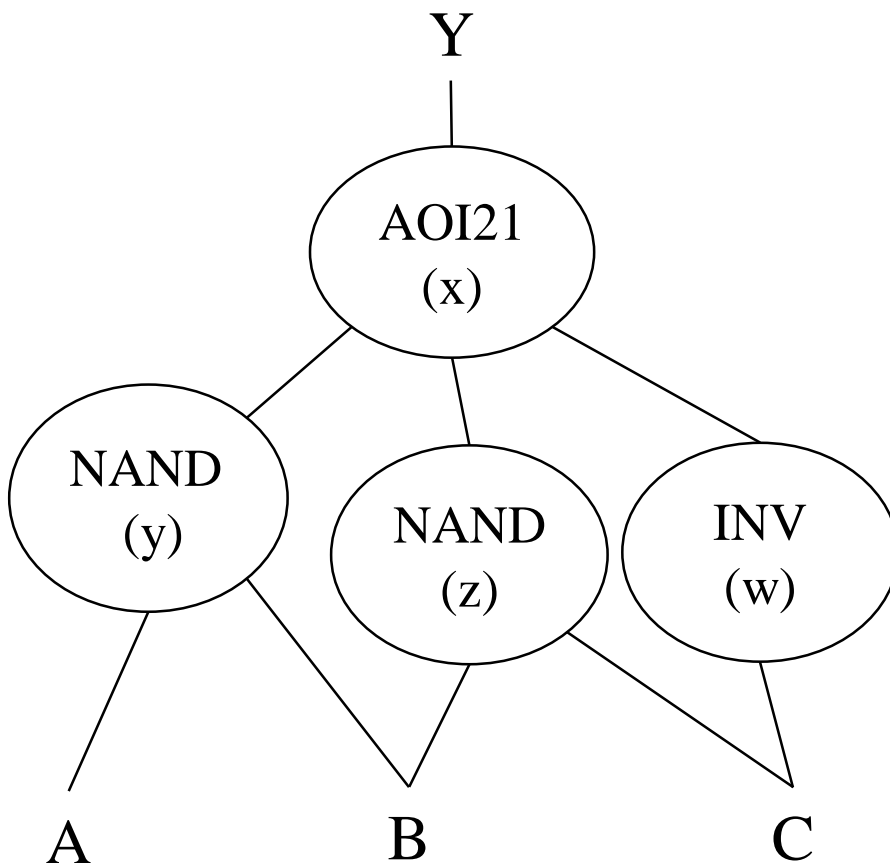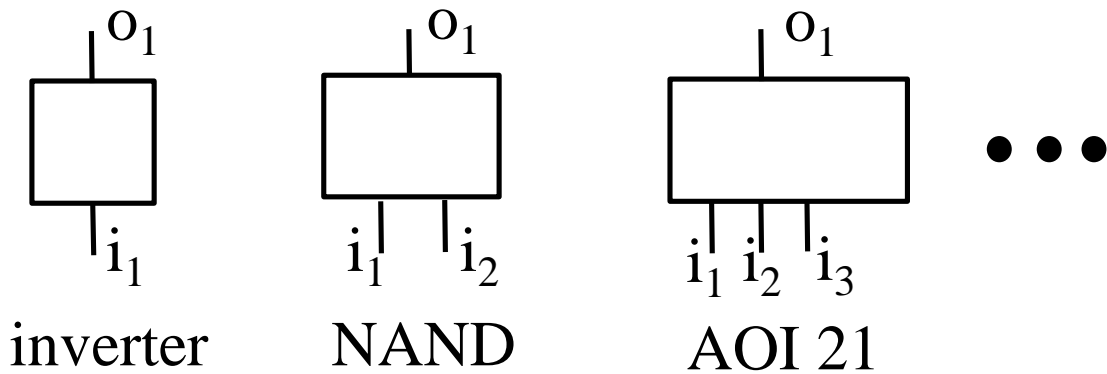



Different Placement

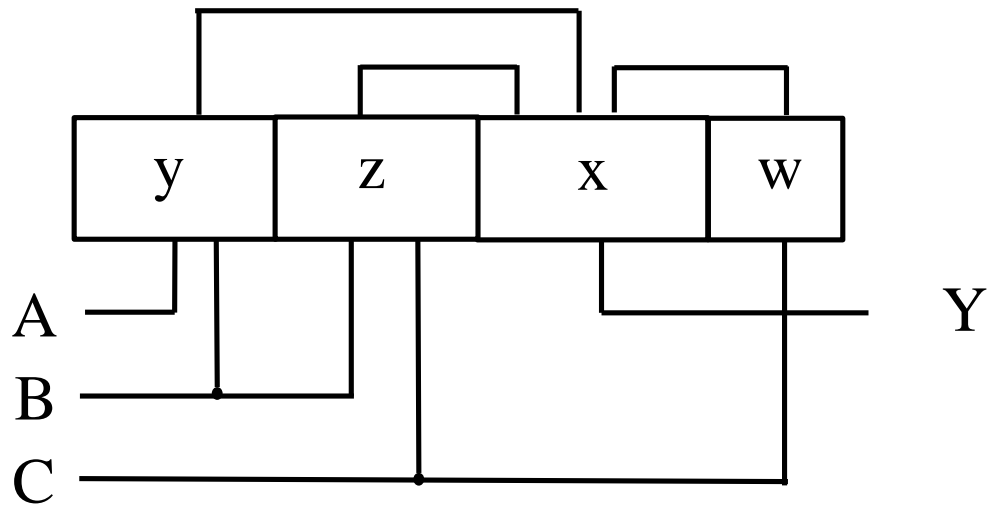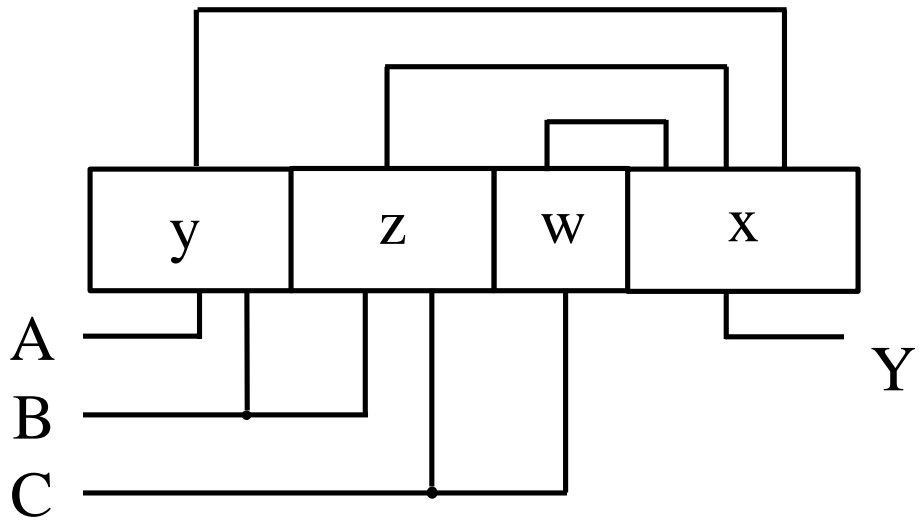

Local Optimization

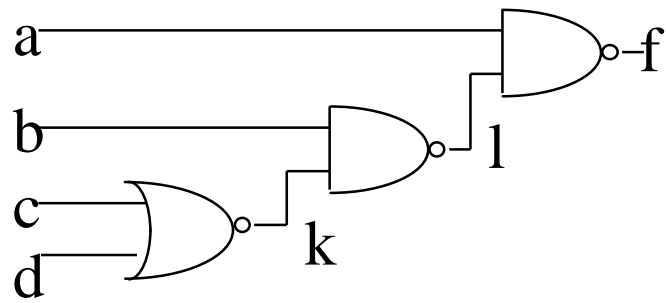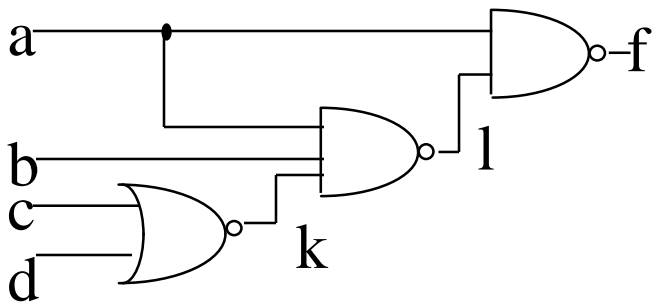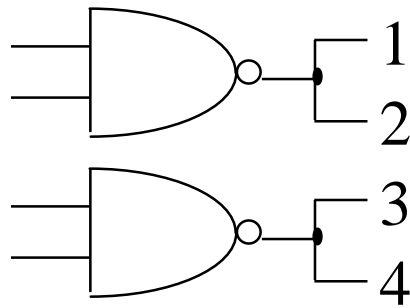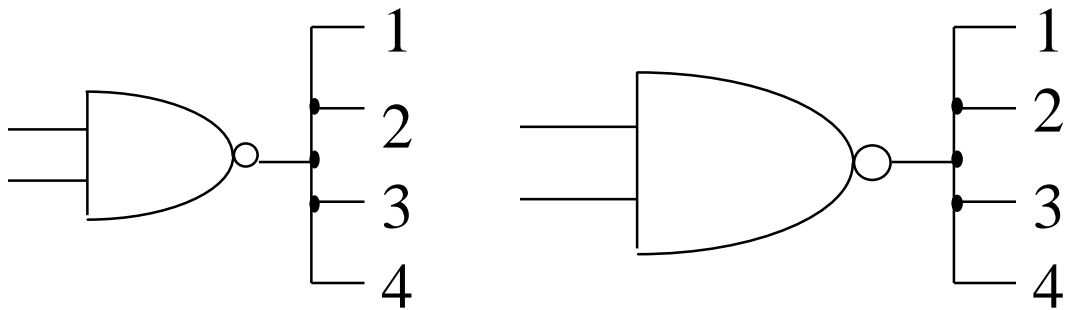

Circuit Restructuring

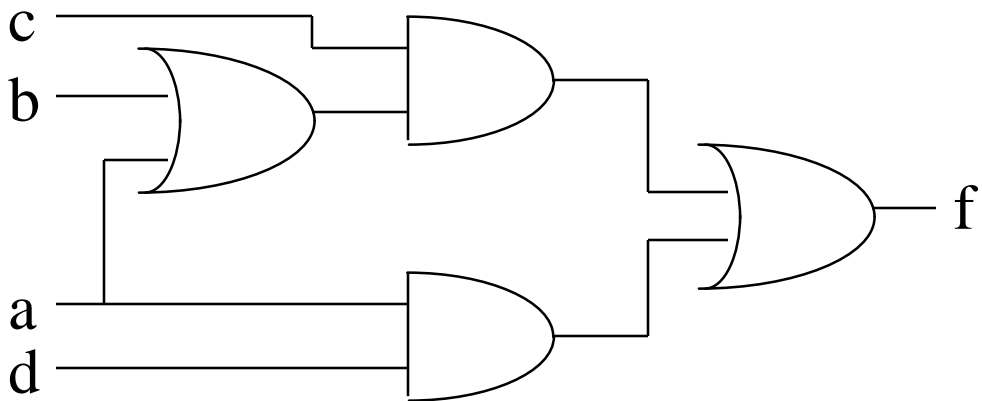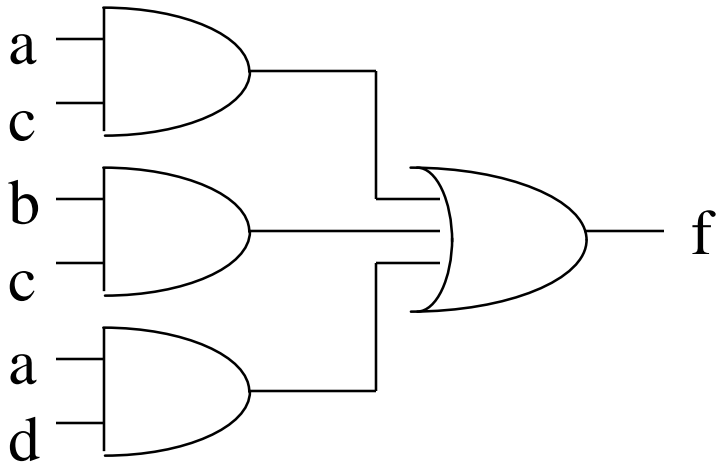

Representation Choices

- How to represent the function?
- How to represent the implementation?


Two-level logic :

two issues are merged

Multi-level logic :

- . merged view (representation and implementation are one)
- . separated view

Boolean Network

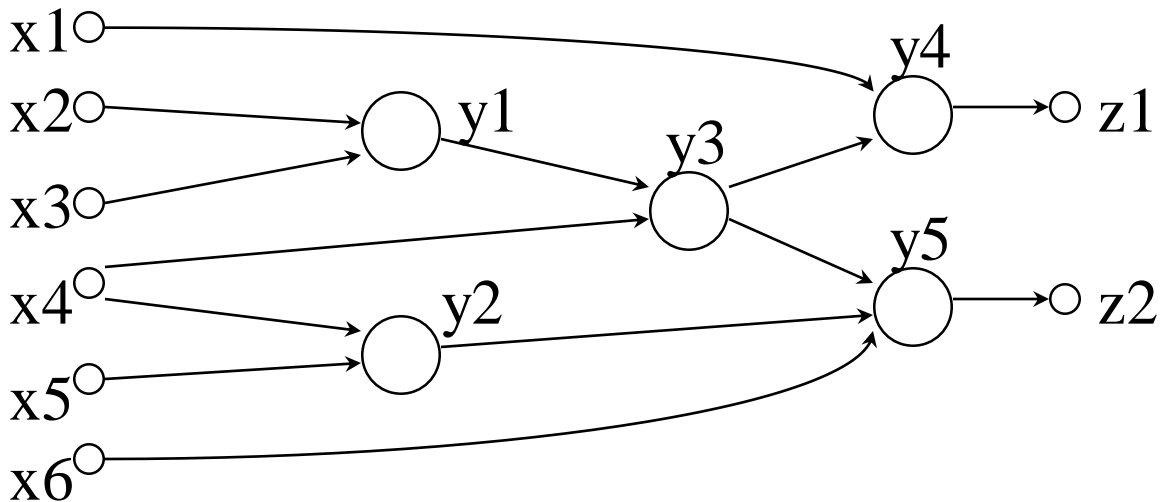

$$y_1 = f_1(x_2, x_3) = x_2' + x_3'$$

$$y_2 = f_2(x_4, x_5) = x_4' + x_5'$$

$$y_3 = f_3(x_4, y_1) = x_4' y_1'$$

$$y_4 = f_4(x_1, y_3) = x_1 + y_3'$$

$$y_5 = f_5(x_6, y_2, y_3) = x_6 y_2 + x_6' y_3'$$

- Directed Acyclic Graph (DAG)
- Primary Input (PI)
- Primary Output (PO)
- Intermediate node : logic function f_i , variable y_i
- Edge
- Fan-in, transitive fan-in
- Fan-out, transitive fan-out

Node Representation

(1) Sum-of-Product

$$abc' + a'bd + b'd' + b'e'f$$

adv :

- easy to manipulate and minimize
- many algorithms available

disadv:

- not representative of logic complexity

$$f = ad + ae + bd + be + cd + ce$$

$$f' = a'b'c' + d'e'$$

- not easy to estimate if logic becoming simpler

Node Representation

(2) factored form : Any depth of sum of product

Ex: a


a'

ab'c

ab+c'd

(a+b)(c+a'+de)+f

Node Representation

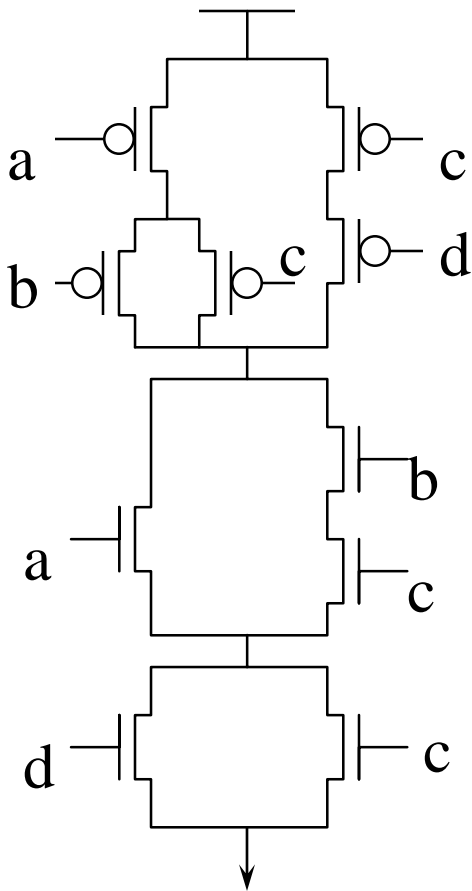

A CMOS complex gate
implementing
 $f = ((a+bc)(c+d))'$

$2 * \text{literal count} = \text{transistors\#}$

adv:


- natural multi-level representation
- good estimate of the complexity of function
- represent both the function and its complement

disadv:

- more difficult to manipulate than two-level form
- lack of the notion of optimality

Node Representation

(3) NAND or NOR form

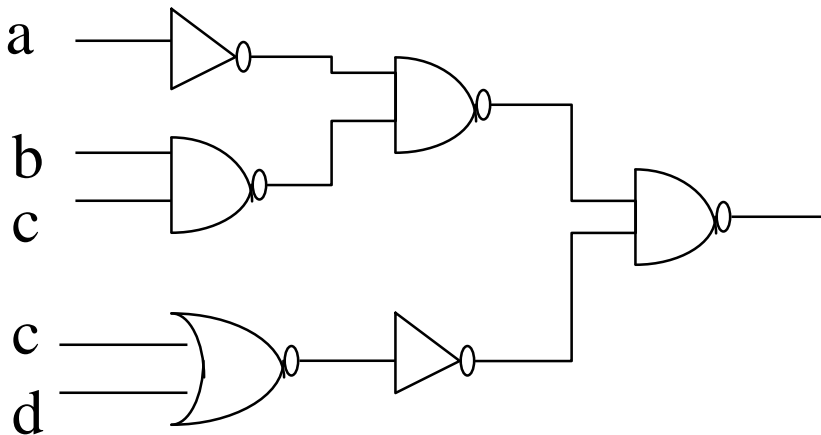

A simple gate implementation of
$$f = ((a+bc)(c+d))'$$

adv :

- simple data structure
storage -save
fast simulation
- efficient optimization strategies for rule-based logic optimization
- complete with inverter count

disadv:

- The network is finely decomposed in a particular way and this may obscure some natural structures.

Multi-level Logic Optimization

■ Technology independent

- Decomposition/Restructuring

Algebraic (Boolean) (SIS)

Functional

- Node optimization

■ Technology dependent

- Technology mapping

Technology Independent Phase

- Restructuring

Basic Operations:

1. decomposition (single function)

$$f = abc + abd + a'c'd' + b'c'd'$$



$$f = xy + x'y'$$

$$x = ab$$

$$y = c + d$$

2. extraction (multiple function)

$$f = (az + bz')cd + e$$

$$g = (az + bz')e'$$

$$h = cde$$



$$f = xy + e$$

$$g = xe' \quad h = ye$$

$$x = az + bz' \quad y = cd$$

Technology Independent Phase

3. factoring (series-parallel decomposition)

$$f = ac+ad+bc+bd+e$$



$$f = (a+b)(c+d)+e$$

4. substitution

boolean

$$g = a+b$$

$$x + x' = 1$$

$$f = a+bc$$

$$x \cdot x' = 0$$

$$(a+b)(a+c)$$

$$f = g(a+c)$$

$$=a+ac+ba+cb$$

5. collapsing

$$f = ga+g'b$$

$$g = c+d$$



$$f = ac+ad+bc'd'$$

$$g = c + d$$

“Division” plays a key role in all these operations.

Division

Division plays a key role in all restructuring operations

- Boolean divide
- Algebraic divide

Algebraic and Boolean Operations

- Algebraic operations:
 - Algebra of expression involving real numbers
 - Those rules that are common to the algebra of real numbers and Boolean Algebra
- Boolean operations:
 - All laws of Boolean Algebra

Boolean Algebra

- Rules hold for Boolean Algebra only
 - Idempotency
$$a \cdot a = a^2 \quad (\text{real number})$$
$$a \cdot a = a \quad (\text{Boolean Algebra})$$
 - Complementation
No direct correspondence in real field
 - Distributivity of “+” over “ \cdot ”
$$a + bc = (a+b)(a+c) \text{ in Boolean Algebra}$$

Not in real number
 - Absorption
$$a + ab = a \text{ in Boolean Algebra}$$

Not in real number

Boolean Divide

- Def 1: p is a Boolean divisor of f if $q \neq \phi$ and r exists such that

$$f = pq + r$$

(p is said to be a factor of f if $r = \phi$)

(1) q is called the quotient , f/p

(2) r is called the remainder

(3) q and r are *not unique*


Let $\overline{f} = (f, d, r)$

- Def 2 : g is a Boolean divisor of f if there exists h such that
$$f \subseteq gh + e \subseteq f + d \quad (d : \text{don't care})$$

Boolean Divide


- Theorem 1

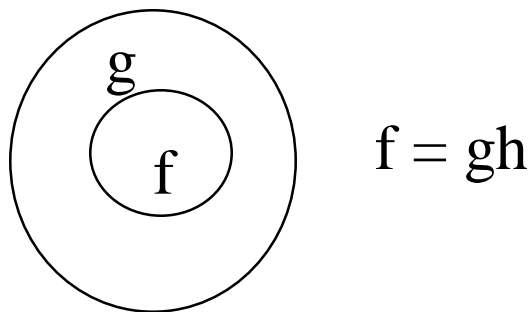A logic function g is a Boolean factor of a logic function of $f \iff f \subseteq g$



- Theorem 2

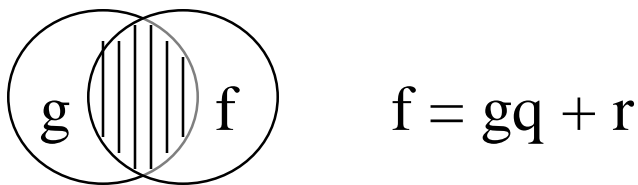If $f \bullet g \neq \phi$, then g is a Boolean divisor of f .



too many Divisor (factors)!

Algebraic Divide

- Def 3:

f is an algebraic expression if f is a set of cubes such that no one cube contains another.

Ex: $a + ab$ is not an algebraic expression because a contains ab .

$ab + bd$ is an algebraic expression

- Def 4:

$f \bullet g$ is an algebraic product if f and g are algebraic expression and have disjoint support (no input variable in common). Otherwise,

$f \bullet g$ is a Boolean product.

Ex:

$(a+b)(c+d) = ac+ad+bc+bd \Rightarrow$ Algebraic product

$(a+b)(a+c) = aa+ac+ba+bc \Rightarrow$ Boolean product

Weak Division

Given f and p , return q and r such that pq is an algebraic product and

$$f = pq + r$$

Algebraic Divide

- Weak-Div (f, p)

U = set {U_j} of cubes in f with literals
not in p deleted

$V = \text{set } \{V_j\}$ of cubes in f with literals in P deleted

$$\mathcal{U}^i = \{V_j \in V : U_j = p_i\}$$

$$\mathbf{q} = \bigcap \mathcal{U}^i$$

$$\mathbf{r} = \mathbf{f} - \mathbf{p}\mathbf{q}$$

Ex:

$$f = ac + ad + ae + bc + bd + be + a'b$$

p = a + b

$$U = a + a + a + b + b + b + b$$

$$V = c + d + e + c + d + e + a'$$

$$\mathcal{U}^a = \mathbf{c} + \mathbf{d} + \mathbf{e}$$

$$\mathbf{u}^b = \mathbf{c} + \mathbf{d} + \mathbf{e} + \mathbf{a},$$

$$q = \mathcal{U}^a \cap \mathcal{U}^b = c + d + e \quad r = f - pq = a'b_{23}$$

Division

- Substitution : knows divisor ? Yes
- Extraction : knows divisor ? No
- Factor : knows divisor ? No
- Decomposition : knows divisor ? No

Boolean Division

- Theorem

$f_1 = hx + e$ be a cover of an incompletely specified function (f, d, r) . Suppose

$$x'g + xg' \subseteq d$$

where g is any function. Then, $f_2 = hg + e$ is also a cover.

- Algorithm

1. $f = h \cdot g + e$ (where $h = f/g$)

2. use a new variable x to represent g ,

$$f = h \cdot x + e$$

3. form the don't care set, $xg' + x'g$


4. minimize f with the don't care

5. quotient f/x (quotient = the terms of f with x)

remainder = the terms of f
without x)

Substitution

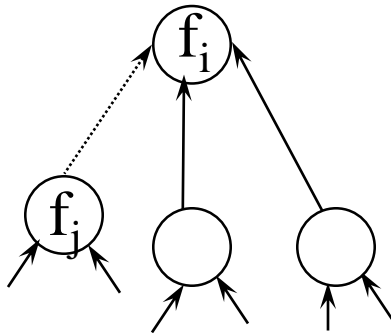- An existing node in a network may be a useful divisor in another node.



Algebraic Substitution

- Dividing the function f_i at node i by f_j or f_j' at node j pair-wise.
- If f_j is a divisor of f_i
$$f_i = g \cdot f_j + r$$

No need to try all pairs

(Cases where f_j is not an algebraic divisor of f_i)

1. f_j contains a literal not in f_i
2. f_j contains more terms than f_i
3. for any literal, the count in f_j exceed that in f_i
4. f_i is f_j 's transitive fan-in (cycle)

Boolean Substitution

- Ex:

$$f = a + bc$$

$$g = a + b$$

substituting g into f (Let $X = a + b$)

$$DC = X(a + b)' + X'(a + b)$$

minimize $(a + bc) \cdot DC'$ (force X to appear in f)

$$\Rightarrow (a + bc)(X(a + b)' + X'(a + b))'$$

$$\text{using Don't Care} = X(a + b)' + X'(a + b)$$

- A minimum cover is $a + bc$. But it does not contain X or X'
- force X (or X') to remain in f
 $\Rightarrow f = a + Xc$

$$f = a + gc$$

$$g = a + b$$

Division

- Substitution : knows divisor ? Yes
- Extraction : knows divisor ? No
- Factor : knows divisor ? No
- Decomposition : knows divisor ? No

Kernel

- Kernel : for finding divisor (algebraic)
 - What is kernel?
 - Kernel algorithm
 - kernel intersection
- Too many divisor, but much smaller number of kernel.

Kernel

- Definition:

An expression is cube-free if no cube divides the expressions evenly.

Ex:

$a + bc$ is cube-free

$ab + ac$ is not cube-free

abc is not cube-free

- Definition:

The kernel of an expression f are the set of expression

$$\mathbf{K}(f) = \{ f/c \mid f/c \text{ is cube free and } c \text{ is a cube} \}$$

Ex:

$f = acb + acd + e$ a kernel

$f/a = cb + cd$ not a kernel

$f/ac = b + d$ a kernel

Kernel

- Definition :

A cube c used to obtain the kernel $k=f/c$ is a co-kernel $c(f)$ denotes the set of co-kernel.

Ex:

$$\begin{aligned} f &= adf + aef + bdf + bef + cdf + cef + g \\ &= (a + b + c)(d + e)f + g \end{aligned}$$

kernel	co-kernel
$a+b+c$	df,ef
$d+e$	af,bf,cf
$(a+b+c)(d+e)$	f
$(a+b+c)(d+e)f+g$	1

Kernel

- Theorem:

f and g have a common multiple-cube divisor d

$$\Leftrightarrow \exists \quad h_f \in \mathcal{K}(f) \quad h_g \in \mathcal{K}(g) \\ \text{such that } d = h_f \cap h_g$$

Ex:

$$f_1 = ab (cl + f + g) + m$$

$$f_2 = ai (cl + f + j) + k$$

$$\mathcal{K}(f_1) = \{ cl + f + g \}$$

$$\mathcal{K}(f_2) = \{ cl + f + j \}$$

$$\mathcal{K}(f_1) \cap \mathcal{K}(f_2) = cl + f$$

common multiple cube divisor $cl + f$

Kernel

- The level of a kernel

A kernel is level-0 if it has no kernels except itself.

A kernel is level-n if it has at least one level n-1 kernel but no kernel (except itself) of level n or higher.

Ex:

$$f = (a+b+c)(d+e)f + g$$

kernel	level
$a+b+c$	0
$d+e$	0
$(a+b+c)(d+e)$	1
$(a+b+c)(d+e)f + g$	2

Kernel

- Why need to define level of kernel?
 - sometimes it is nearly as effective to compute a certain subset of kernel
 - computation time and quality trade off

Kernel Algorithm

Kernel(j \downarrow literal index, g \downarrow expression)

$R = \phi$

for ($i=j$; $i \leq n$; $i++$) {

 if (l_i appears in more than one cube)

$c =$ largest cube dividing $g/\{l_i\}$ evenly

 if ($l_k \notin c$ for all $k < i$)

$R = R \cup \text{Kernel}(i+1, g/(\{l_i\} \cup c))$

 }


$R = R \cup \{g\}$

Return R

- The literals in the support of f are numbered from 1 to n .

Kernel Algorithm
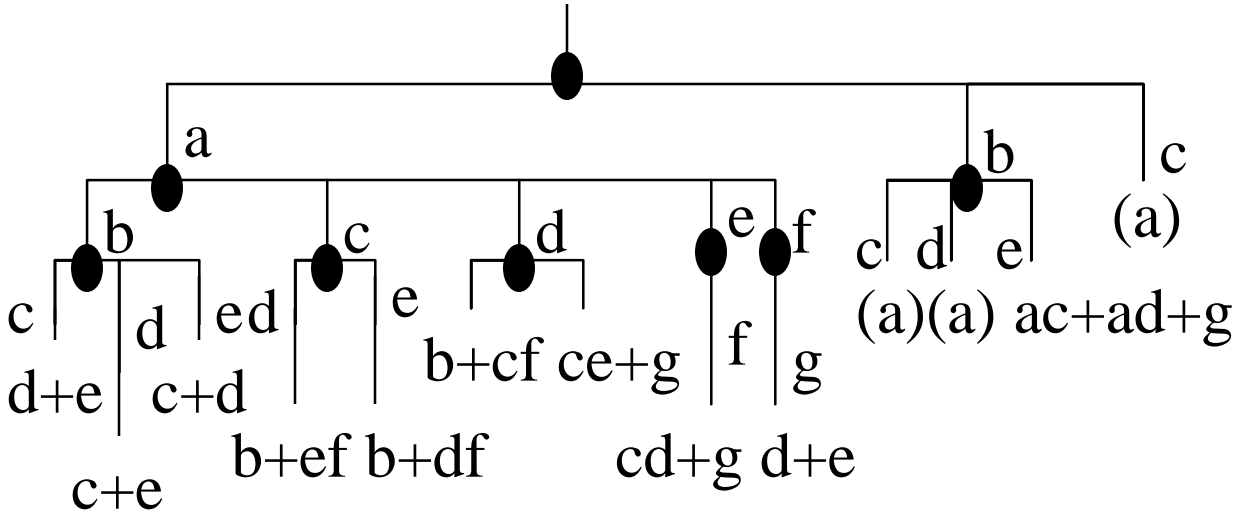
$$f = abcd + abce + adfg + aefg + abde + acdef + beg$$



co-kernel	kernel
1	$a((bc+fg)(d+e)+de(b+cf))+beg$
a	$(bc+fg)(d+e)+de(b+cf)$
ab	$c(d+e)+de$
abc	$d+e$
abd	$c+e$
abe	$c+d$
ac	$b(d+e)+def$
acd	$b+ef$

Note : $f/bc = ad+ae = a(d+e)$.

Kernel Intersection

- Kernel Intersection

$$K = \{ K_1, K_2, \dots, K_n \}$$

- Form a new expression $IF(k)$ which corresponds to the set K of kernel
 - associate each distinct cube with a new literal
 - each kernel corresponds to a cube of the new function
 - Then, every element in the set of co-kernel of $IF(K)$ corresponds to a unique kernel intersection.

Example

Ex:

Let $t_1 = abc$

$t_2 = de$

$t_3 = fg$

$t_4 = fh$

$t_5 = gh$

$$K_1 = abc + de + fg = t_1 t_2 t_3$$

$$K_2 = abc + de + fh = t_1 t_2 t_4$$


$$K_3 = abc + fh + gh = t_1 t_4 t_5$$

$$\text{IF}(K) = t_1 t_2 t_3 + t_1 t_2 t_4 + t_1 t_4 t_5$$

$$\text{Co-kernel of } (\text{IF}(k)) = \{t_1, t_1 t_2, t_1 t_4\}$$

Kernel Extraction

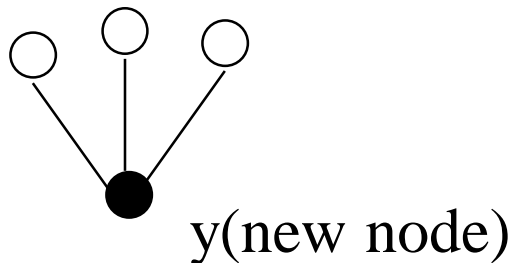- Kernel extraction (k, n)
 1. Find all kernels of all functions and generate all kernel intersections.
 2. Choose one with best “value” .
 3. Create a new node with this as function.
 4. Algebraically substitute new node everywhere.
 5. Repeat 1,2,3,4 until value \leq threshold.
- Step1: Selection of level of kernel determines speed and quality trade off.
- Step2:



$$\text{area-value}(y) = \text{freq}(y) * \text{literal}(y) - \text{literal}(y) - \text{freq}(y)$$

Factor

- Factor(F)
 1. If $|F| = 1$ return False
 2. $D = \text{Choose_Divisor}(F)$
 3. $(Q,R) = \text{Divide}(F,D)$
 4. Return. $\text{Factor}(Q)*\text{Factor}(D) + \text{Factor}(R)$
- Efficiency and quality
 - Step2 :
 - Divisor : 1. choose literal factor
 - 2. choose one level-0 kernel
 - 3. choose the best kernel
 - Step3 :
 - Algebraic divide
 - Boolean divide

Decomposition

- Decomposition
 - similar to factoring, except that each divisor is formed as a new node
 - For each method of factoring, we have the associated method for decomposition.

Example

Ex: $f_1 = ab(c(d+e)+f+g)+h$

$$f_2 = ai(c(d+e)+f+j)+k$$

– extraction(level-0 kernel)

$$\alpha^0(f_1) = \{d+e\}$$

$$\alpha^0(f_2) = \{d+e\}$$

$$\alpha^0(f_1) \cap \alpha^0(f_2) = \{d+e\}$$

$$l = d + e$$

$$f_1 = ab(cl+f+g)+h$$

$$f_2 = ai(cl+f+j)+k$$

– extraction (level-0 kernel)

$$\alpha^0(f_1) = \{cl+f+g\}$$

$$\alpha^0(f_2) = \{cl+f+j\}$$

$$\alpha^0(f_1) \cap \alpha^0(f_2) = \{cl+f\}$$

$$m = cl+f \quad l = d+e$$

$$f_1 = ab(m+g)+h$$

$$f_2 = ai(m+j)+k$$

No kernel intersection at
this point

Example (cont.)

– cube extraction


$$n = am$$

$$m = cl+f$$

$$l = d+e$$

$$f1 = b(n+ag)+h$$

$$f2 = i(n+aj)+k$$

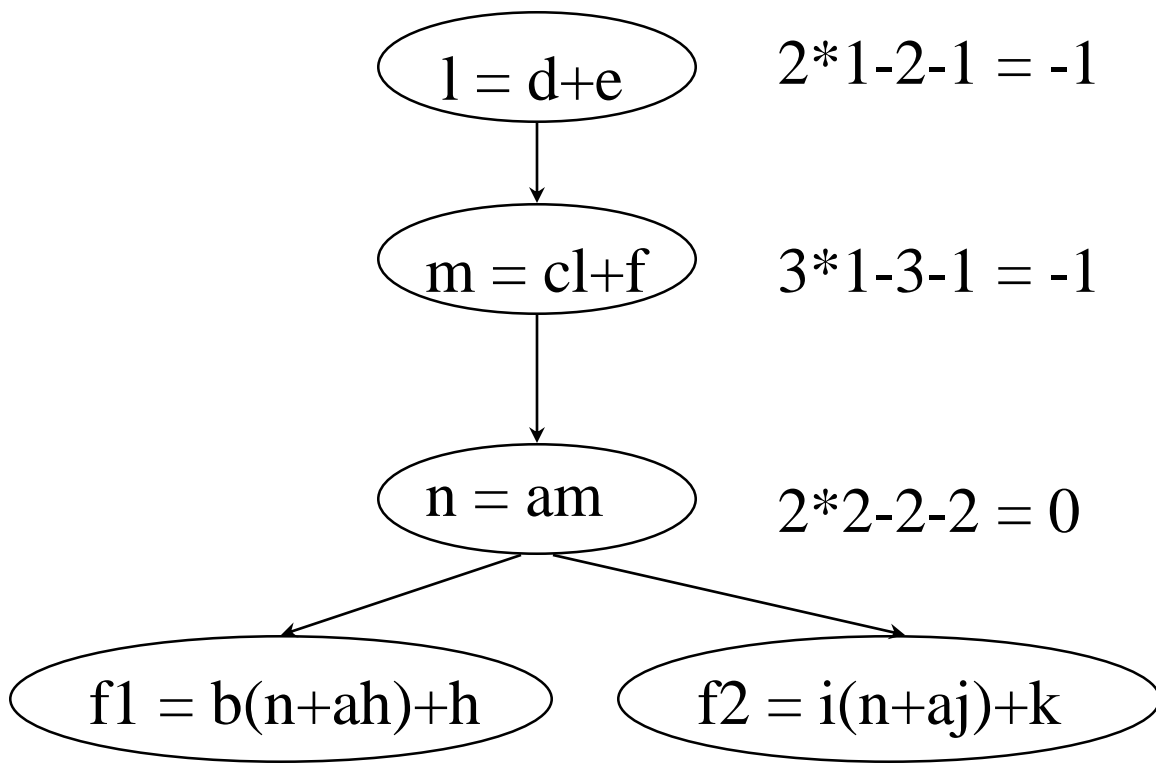

Example (cont.)

- eliminate -1 (collapsing)

