

Multi-Level Logic Optimization - Node Optimization

Simplification

- Represent each node in two level form
- Use espresso to minimize each node
- Several simplification procedures which vary only in the size of don't care constructed
 - don't care set empty
 - subset of don't care

Simplification

Don't care

- External DC
- Internal DC (derived from the structure)
 - (1) Satisfiability DC (SDC)
 - (2) Observability DC (ODC)

Satisfiability Don't Care

- Satisfiability DC (to all nodes)

Ex: $x = ab$

$$y = a'b'$$


$$f = x'y' + a$$

$$\therefore x \oplus ab = x(ab)' + x'(ab)$$

- Why?

Expand the Boolean space of PI to include intermediate variables $B^n \rightarrow B^{n+m}$

$n=2 \ m=1$

 

In general, $SDC = \sum (y_i \cdot f_i' + y_i' \cdot f_i)$

Observability Don't Care

- Observability DC (to certain intermediate node)

$\frac{\delta f}{\delta x}$ f is sensitive to the value of x

$(\frac{\delta f}{\delta x})'$ f is not sensitive to the value of x
x is observable at f if $\frac{\delta f}{\delta x} \neq 0$

(Note $\frac{\delta f}{\delta x}$ is a function of the inputs)


Example

Ex:

$$u = ab + xc' + x'b'$$

$$x = a'b + ac'$$
 
$$\left(\frac{\delta u}{\delta x}\right)' = u_x \bullet u_{x'} + u_x' \bullet u_{x'}$$



$$u_x = ab + c'$$

$$u_{x'} = ab + b'$$

$$\begin{aligned} \left(\frac{\delta u}{\delta x}\right)' &= u_x \bullet u_{x'} + u_x' \bullet u_{x'}' \\ &= (ab + b'c') + a'b'c \quad (\text{the ODC of } x) \end{aligned}$$

$$u = ab + xc' + x'b'$$

$$a=1 \ b=1 \quad \Rightarrow u = 1 \cdot 1 + xc' + x'b' = 1$$

$$b=0 \ c=0 \quad \Rightarrow u = a \cdot 0 + x \cdot 1 + x' \cdot 1 = 1$$

$$a=0 \ b=1 \ c=1 \quad \Rightarrow u = 0 \cdot 1 + x \cdot 0 + x' \cdot 0 = 0$$

Observability Don't Care

- ODC relative to x is

$$\text{ODC}_x = \prod_{f_i \in \text{output}} \left(\frac{\partial f_i}{\partial x} \right)'$$

- Including the external DC

$$\prod_{f_i \in \text{output}} \left(\left(\frac{\partial f_i}{\partial x} \right)' + D_{xi} \right)$$

- In general, the complete DC is too large
solutions:

filter the DC


=> subset “support” filter

Controlling and Non-controlling Values of Simple Gates


- Given a **simple gate** (i.e. AND, OR, NAND, NOR), a **controlling** value on an input determines the output of the gate independent of the other inputs
- Given a **simple gate** (i.e. AND, OR, NAND, NOR), a **non-controlling** value on an input cannot determine the output of the gate independent of the other inputs
- Example:
 - 0 is a controlling value for AND gate
1 is non-controlling value for AND gate
 - 0 is a controlling value for NAND gate
1 is non-controlling value for NAND gate
 - 1 is a controlling value for OR gate
0 is non-controlling value for OR gate
 - 1 is a controlling value for NOR gate
0 is non-controlling value for NOR gate

Boolean Difference of Simple Gates

 - Non-controlling value of a side input is merely a specialization of the Boolean difference of an on-input to the simple gate
- a is an on-input and b is a side input



$$\frac{\partial f}{\partial a} = b$$

 

$$\frac{\partial g}{\partial a} = \bar{b}$$


ODC of Simple Gates

- Controlling value of a side input is merely a specialization of ODC of an on-input to the simple gate
- a is an on-input and b is a side input




- ODC = complement of Boolean difference

 Example of Computing Boolean Difference of *ff*



- $(C = 0 \text{ and } D=x) \text{ or } (C = x \text{ and } D=0)$
 $\Rightarrow C' + D'$
- $E = 1$
 $\Rightarrow E$
- Boolean Difference (*ff*) = $(C' + D') E$
(conditions of side inputs are *anding*)

Example of Computing ODC of *ff*

 

- $(C = 1 \text{ and } D=1)$
 $\Rightarrow CD$
- $E = 0$
 $\Rightarrow E'$
- $ODC(ff) = CD + E'$ (conditions of side inputs are *oring*)
- $(ODC(ff))' = \text{Boolean Difference } (ff)$
 $= (C' + D')E$

Standard Script of MisII

sweep constant propagation, remove buffer
eliminate -l collapse; node has < 1000 cubes
simplify espresso for each node
eliminate -l

sweep
eliminate 5 value > 5
simplify

resub -a algebraic div
gkx -abt 30 -a generate all kernel -b the best kernel inter
 -t value saved


resub -a; sweep
gcx -bt 30 -b the best cube -t the value saved
resub -a; sweep

gkx -abt 10
resub -a; sweep
gcx -bt 10
resub -a; sweep

.....

Incompleteness of Don't Cares

- Example

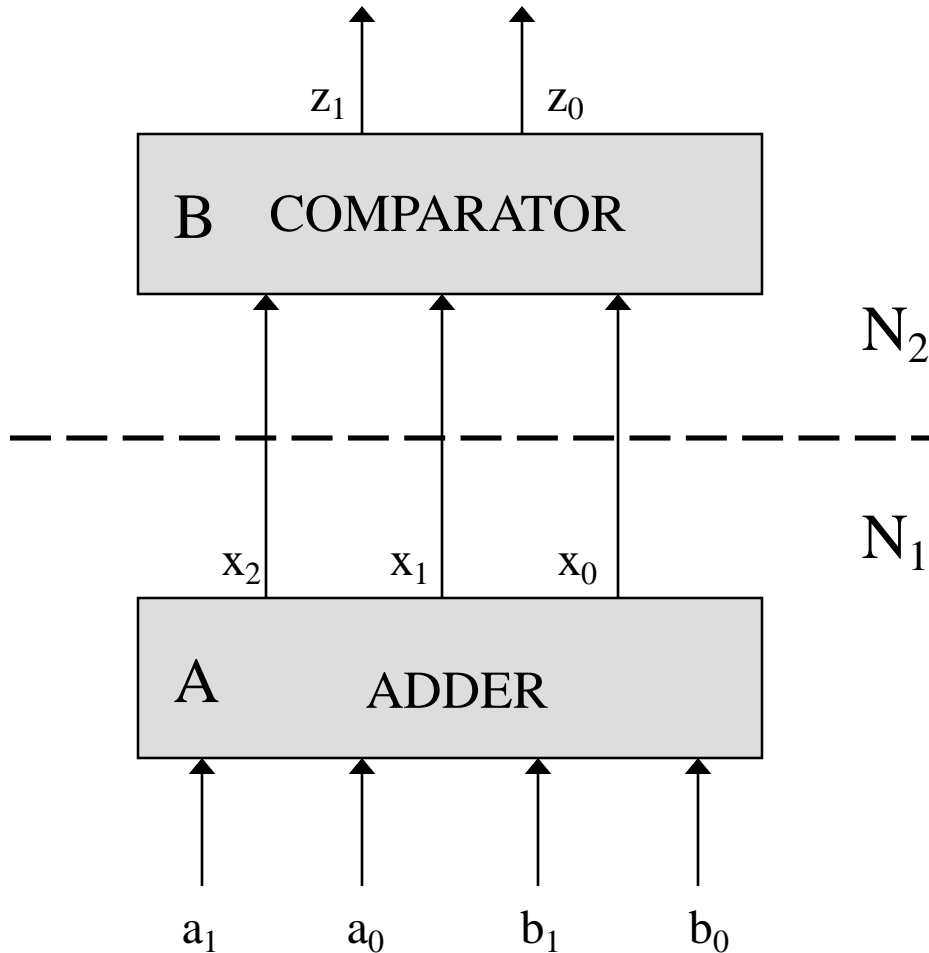

$$Z = 01 \Rightarrow a + b < 3$$

$$Z = 00 \Rightarrow a + b = 3$$

$$Z = 10 \Rightarrow a + b > 3$$

Equivalence

x_2	x_1	x_0	z_1	z_0
0	0	0	0	1
0	0	1	0	1
0	1	0	0	1
0	1	1	0	0
1	0	0	1	0
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

Input values 000, 001, and 010 are equivalent with respect to ***B***.

{000,001,010} forms an equivalence class.

The other equivalent classes are:

{011} and {100,101,110,111}

Boolean Relation Formulation

If x' , x'' are input values indistinguishable from the outputs of \mathbf{B} , they are interchangeable output values for \mathbf{A} .

a_1	a_0	b_1	b_0	x_2	x_1	x_0
0	0	0	0	{000,001,010}		
0	0	0	1	{000,001,010}		
0	0	1	0	{000,001,010}		
0	1	0	0	{000,001,010}		
1	0	0	0	{000,001,010}		
0	0	1	1	{011}		
0	1	0	1	{000,001,010}		
0	1	1	0	{011}		
1	0	0	1	{011}		
1	0	1	0	{100,101,110,111}		
1	1	0	0	{011}		
0	1	1	1	{100,101,110,111}		
1	0	1	1	{100,101,110,111}		
1	1	0	1	{100,101,110,111}		
1	1	1	0	{100,101,110,111}		
1	1	1	1	{100,101,110,111}		

Example

The optimal implementation of the following relation $R \subseteq B^2 \times B^2$

a	b	x	y
0	0	0 0	0 1
0	1	0 1	1 0
1	1	1 1	
1	0	1 0	


b \ a	0	1
	0	1
0	00	10
1	01	11

b \ a	0	1
	0	1
0	00	10
1	10	11

b \ a	0	1
	0	1
0	01	10
1	01	11

b \ a	0	1
	0	1
0	01	10
1	10	11

Problems

 

1. How to find a multiple-output sub-network ?
2. How to utilize Boolean Relations for minimization ?
 - full set of Boolean Relation
 - subset of Boolean Relation